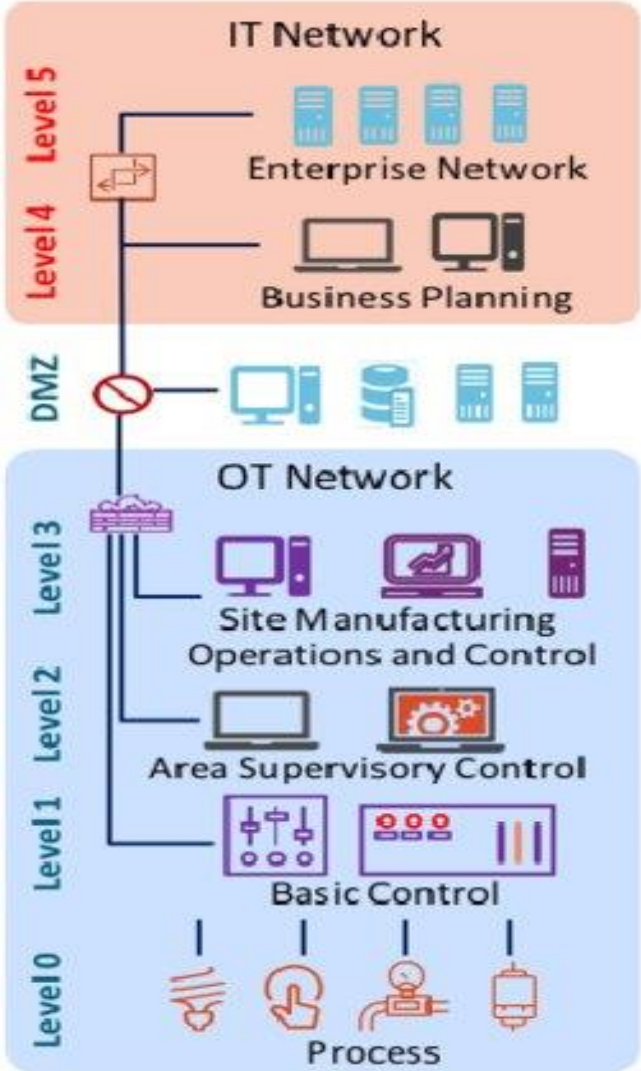


Tutorial 3

Ladder Logic

Basics

IT & ICS Kill chain



Planning	Reconnaissance	
Preparation	Weaponization	Targeting
Cyber Intrusion	Attempt	Delivery
	Success	Exploit
		Install/Modify
Management & Enablement	C2	
Sustainment, Entrenchment Development & Execution	Act	
Attack Development & Tuning	Develop	
Validation	Test	
ICS Attack	Deliver	
	Install/Modify	
	Execute	

First stage : Ladder Logic (diagrammatic notation)


- Diagrammatic Boolean symbols:

Input 1



True → contact ON
False → contact OFF

Input 2

 

True → contact OFF
False → contact ON

First stage : Ladder logic (diagrammatic notation)

output 1

$\left[\begin{array}{c} S \end{array} \right]$



Set output 1 when it is True

output 1


$\left[\begin{array}{c} R \end{array} \right]$




Reset output 1 when it is True

Ladder Logic (Wikipedia)


AND

 

NOT

 

OR

 


[] input () output

 
Example 1: Controlling a Conveyor Belt

Page 262


The following figure shows a conveyor belt that can be activated electrically. There are two push button switches at the beginning of the belt: S1 for START and S2 for STOP. There are also two push button switches at the end of the belt: S3 for START and S4 for STOP. It is possible to start or stop the belt from either end. Also, sensor S5 stops the belt when an item on the belt reaches the end.



Ladder Logic for example 1

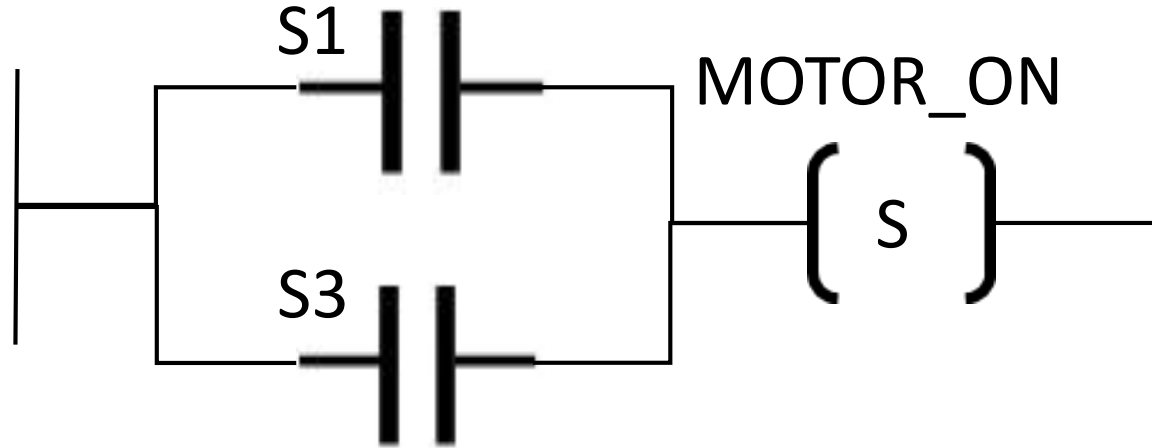

Turn ON the motor belt

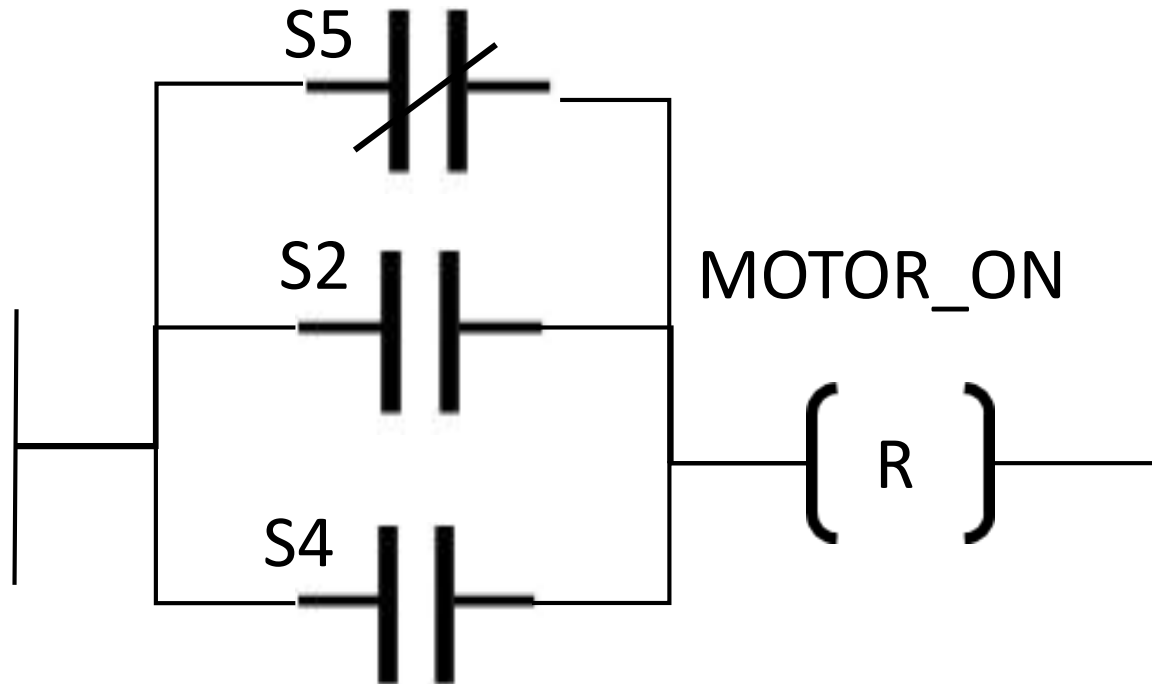

Turn OFF the motor belt

Second stage: Symbolic Programming

- Symbolic Programming codes (From the table at page 261)

Mnemonic	Program Elements Catalog	Description
AW	Word logic instruction	And Word
OW	Word logic instruction	Or Word
CD, CU	Counters	Counter Down, Counter Up
S, R	Bit logic instruction	Set, Reset
NOT	Bit logic instruction	Negate RLO
FP	Bit logic instruction	Edge Positive
+I	Floating-Point instruction	Add Accumulators 1 and 2 as Integer
/I	Floating-Point instruction	Divide Accumulator 2 by Accumulator 1 as Integer
*I	Floating-Point instruction	Multiply Accumulators 1 and 2 as Integers
>=I, <=I	Compare	Compare Integer
A, AN	Bit logic instruction	And, And Not
O, ON	Bit logic instruction	Or, Or Not
=	Bit logic instruction	Assign
INC	Accumulator	Increment Accumulator 1
BE, BEC	Program Control	Block End and Block End Conditional
L, T	Load / Transfer	Load and Transfer
SE	Timers	Extended Pulse Timer

Symbolic Programming for example 1


Symbolic Program	
O	S1
O	S3
S	MOTOR_ON
O	S2
O	S4
ON	S5
R	MOTOR_ON

Example 2: Detecting the Direction of a Conveyor Belt

The following figure shows a conveyor belt that is equipped with two photoelectric barriers (PEB1 and PEB2) that are designed to detect the direction in which a package is moving on the belt. Each photoelectric light barrier functions like a normally open contact.

Q2 : Right sign

Q1 : Lift sign

 

Design a Ladder Logic for this operation using sensors (S1, S2) as inputs, and Q1 and Q2 as outputs.
(you have 20 minutes only)

